

# Introduction to Electronics

## Lecture 02 Review on Circuits Basics

**Dr. Hesham A. Omran**

Integrated Circuits Lab (ICL)



Electronics and Communications Eng. Dept.

Faculty of Engineering

Ain Shams University

# Ohm's Law

---

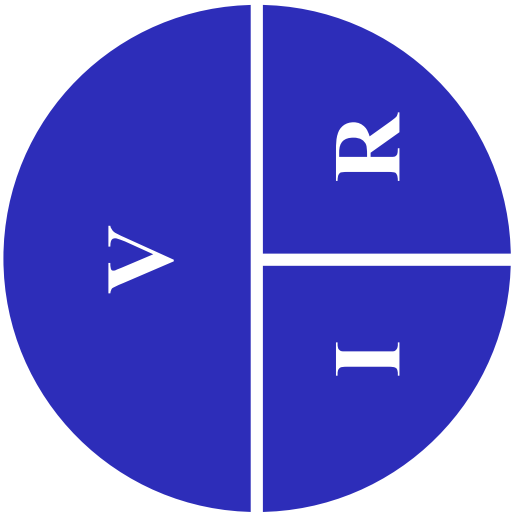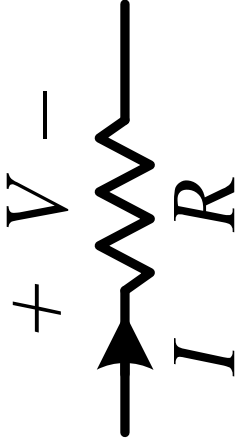

$$V = IR$$

$$I = \frac{V}{R}$$


$$R = \frac{V}{I}$$

# Kirchhoff's Current Law (KCL)

- ❑ The sum of all currents flowing into a node is zero.

$$\Sigma I = 0$$

$$I_1 + I_2 + I_3 - I_4 = 0$$

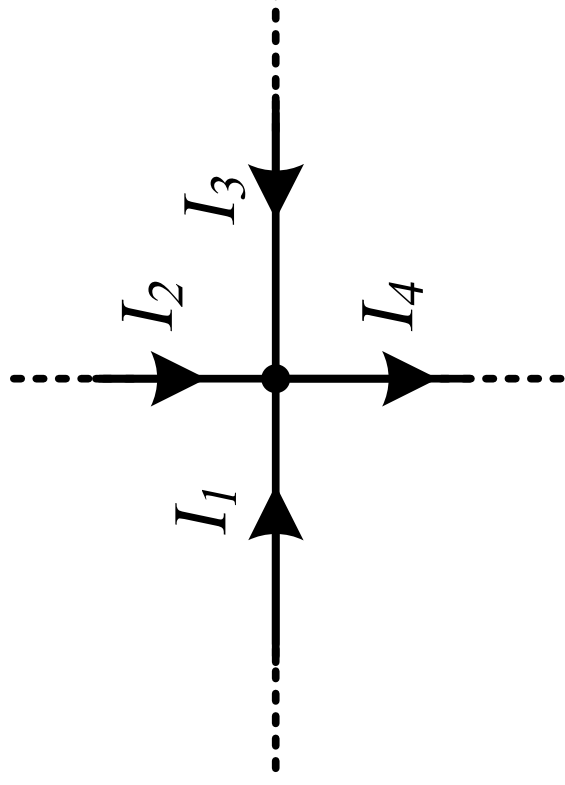


# Kirchhoff's Voltage Law (KVL)

- ❑ The sum of all voltage drops around any closed loop is zero

$$\Sigma V = 0$$

$$-V_{DD} + I_D R_D + V_{DS} + I_D R_S = 0$$
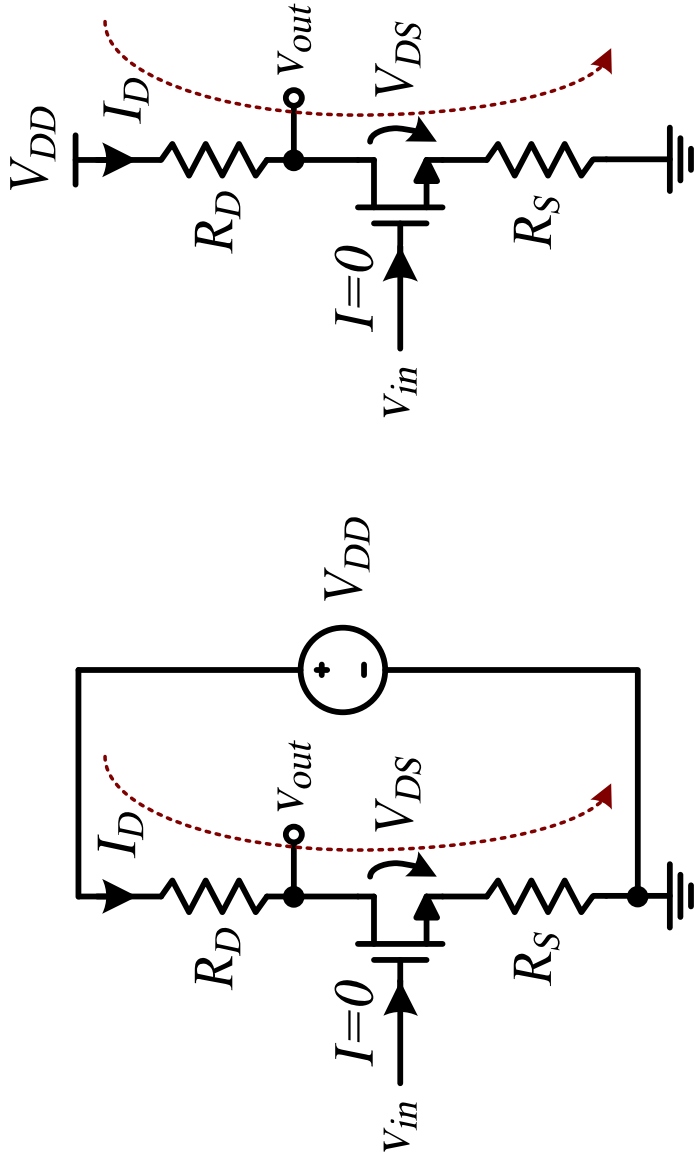
$$V_{DD} = I_D R_D + V_{DS} + I_D R_S = I_D (R_D + R_S) + V_{DS}$$




# Resistor Combinations

- ❑ Resistors in series: Largest resistor dominates



$$R_{eq} = R_1 + R_2 + R_3$$

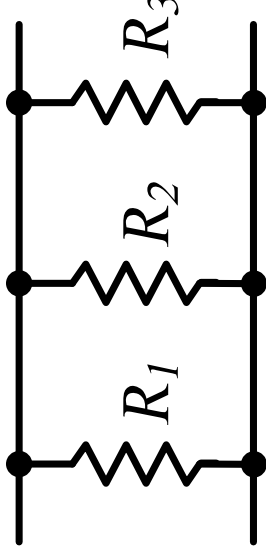- ❑ Resistors in parallel: Smallest resistor dominates




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

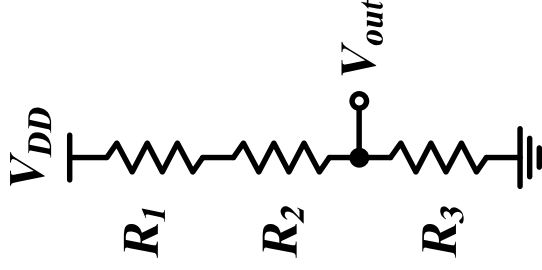
# Voltage and Current Dividers

- ❑ Voltage divider → the largest resistor takes most of the voltage
- ❑ Current divider → the smallest resistor (largest conductance) takes most of the current
  - Remember that current flows in the least resistance path

$$V_{out} = V_{DD} \cdot \frac{R_3}{R_1 + R_2 + R_3}$$


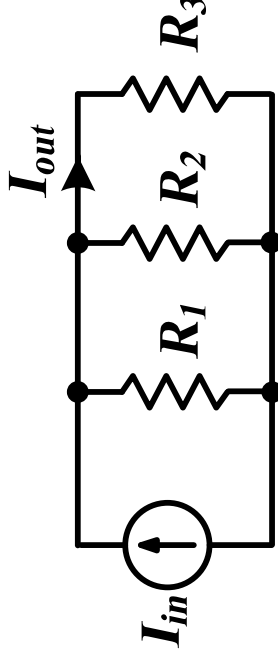
$$I_{out} = I_{in} \cdot \frac{G_3}{G_1 + G_2 + G_3}$$






# Thevenin Equivalent Circuit

- Any one port circuit can be replaced by a voltage source and a series impedance

$$V_{TH} = V_{o.c.}$$

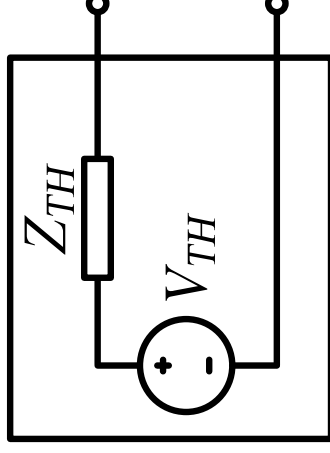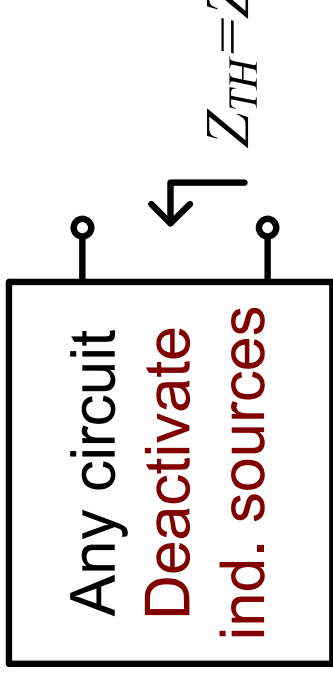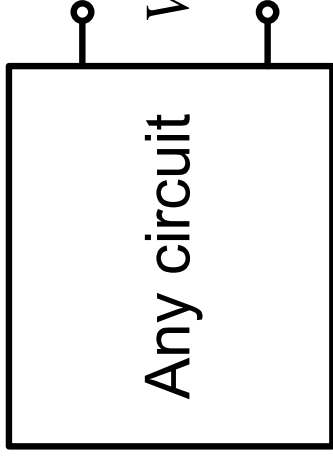$Z_{TH} = Z_{eq}$  (turn OFF all independent sources)



# Norton Equivalent Circuit




- Any one port circuit can be replaced by a current source and a parallel impedance

$$I_N = I_{s.c.}$$

$Z_N = Z_{eq}$  (turn OFF all independent sources)

$$Z_N = Z_{TH}$$

$$V_{TH} = V_{o.c.} = I_N \times Z_N$$

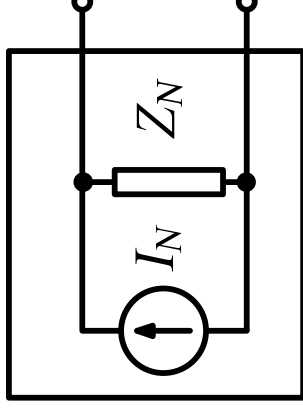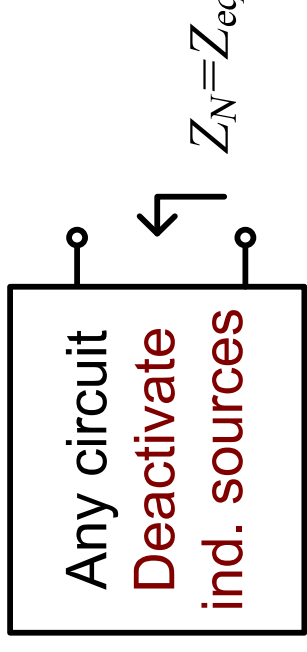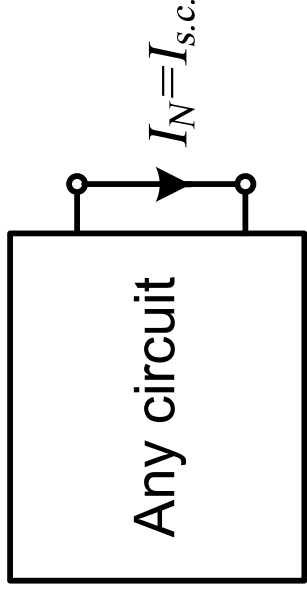



# Superposition Theorem

- ❑ Deactivate all independent sources except one
  - Independent voltage source → short circuit (s.c.)
  - Independent current source → open circuit (o.c.)
  - Do NOT deactivate dependent sources
- ❑ Solve the circuit
- ❑ Repeat the previous two steps for every source
- ❑ Algebraically add all the results

**We use this frequently to separate AC and DC solutions**

# Superposition Theorem




DC + AC

=

DC

+

AC

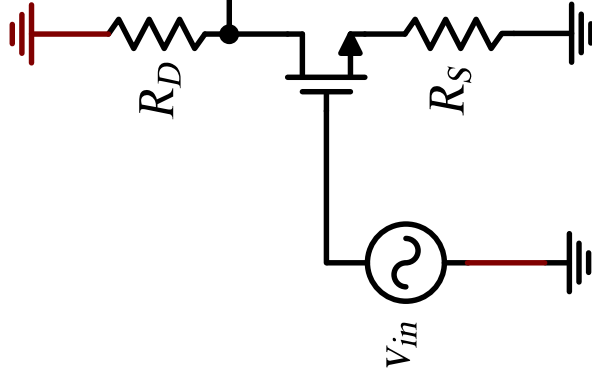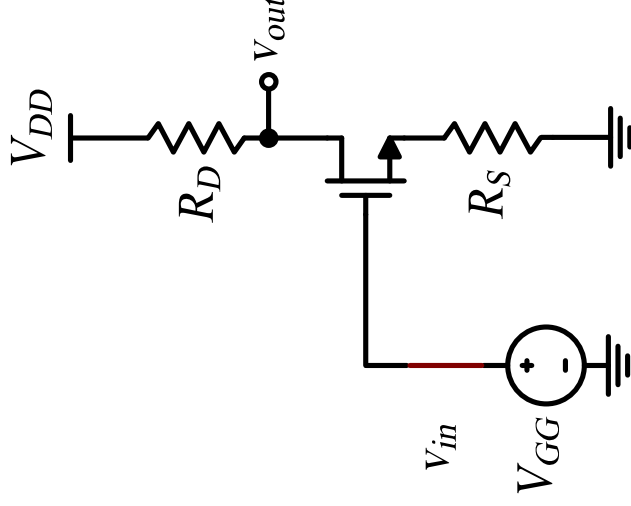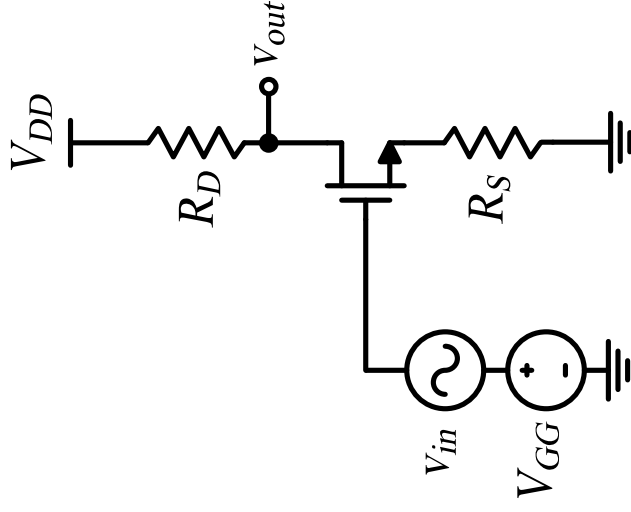

# Capacitance

$$Q = CV \quad \Rightarrow \quad i = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$V = V_o \cos(\omega t + \theta) = V_o \cdot \operatorname{Re}\{e^{j(\omega t + \theta)}\}$$

$$V = V_o e^{j(\omega t + \theta)} = V_o \angle \theta$$

$$i = C \frac{dV}{dt} = j\omega C (V_o e^{j\omega t}) = j\omega C \cdot V$$


$$Z_C = \frac{V}{i} = \frac{1}{j\omega C} = \frac{1}{sC} \Rightarrow X_C = |Z_C| = \frac{1}{\omega C}$$

$$\omega \uparrow \uparrow \Rightarrow X_C \rightarrow 0 \Rightarrow \text{s.c.}$$

$$\omega \downarrow \downarrow \Rightarrow X_C \rightarrow \infty \Rightarrow \text{o.c.}$$

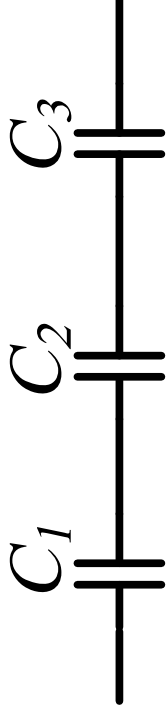
# Capacitance Combinations

- ❑ Capacitors in series: Smallest capacitor dominates



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

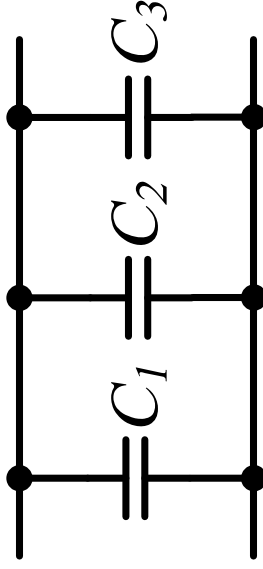- ❑ Capacitors in parallel: Largest capacitor dominates



$$C_{eq} = C_1 + C_2 + C_3$$

---

# Thank you!